

**NC State University**

**Department of Electrical and Computer Engineering**

**ECE 564: ASIC and FPGA Design with Verilog Fall 2021**

**Project: Binary Artificial Neural Network**

**by**

**Zong-Ru Li**

**Unity ID: zli87**  
**Student ID: 200425490**

**Abstract**

Since 2015, binary neural networks have become popular because they require less computing resources and compute faster than traditional neural networks. This project aims to investigate different microarchitecture and synthesis optimization techniques to design a high-performance binary neural network ASIC. To reach the best performance, I compare the result of four binary convolution microarchitectures and five synthesis optimization techniques. My result shows that using parallelized small adders has a faster critical path than using one big adder. Results also reveal that using netlist optimization and removing unnecessary reset registers can shrink the total cell area. However, the final area may be disturbed by logic on non-critical paths. From a safety perspective, this study emphasizes that each process of front-end ASIC has a significant impact on final performance. Besides, this study mentions the need to consider the impact of logic on non-critical paths along with total cell area.

# Table of Contents

---

- **1. Introduction**
- **2. High Level Prototype**
  - 2.1 Discussion of high level modeling
  - 2.2 High Level Synthesis Results
- **3. Interface Specification**
  - 3.1 Top Level Interface
  - 3.2 Signal Description
  - 3.3 SRAM interface timing diagram
  - 3.4 matrix data format
- **4. Micro-Architecture**
  - 4.1 Finite State Machine and Data flow
  - 4.2 Four Different Binary Convolution microarchitecture
- **5. Verification**
  - 5.1 Generate test pattern
  - 5.2 Test Environment
- **6. Synthesis Results Achieved**
  - 6.1 My Synthesis flow
  - 6.2 Synthesis Steps
  - 6.3 Techniques for Performance Area Optimization
- **7. Simulation Result**
- **8. Conclusions**

# 1. Introduction

---

- In this project, I implement a single stage of an all binary convolutional neural network. All the weights and input data are binary. They take on values of -1 and 1, which are represented by 0 and 1, respectively. My design reads the input matrix and weight matrix from two SRAMs, and it writes the output matrix to another SRAM. The size of the weight matrix is fixed at 3x3. Besides, the size of the input matrix has three options: 16x16, 12x12, 10x10.
- Compared with traditional 2-d convolution, binary convolution consume fewer resource and compute faster.
- I will introduce four different microarchitectures of binary neural network(BNN) accelerator. Also, I will discuss five different synthesis optimization techniques and analysis the trade-off of each optimization.

## 2. High Level Prototype

---

### 2.1 Discussion of high level modeling

- BNN.h

```
#include <ap_int.h>

#define WORDSIZE 16 // bits per word
#define uint16 unsigned int

typedef ap_uint<16> bit16;
typedef ap_uint<9> bit9;
typedef ap_uint<6> bit6;
typedef ap_uint<4> bit4;
typedef ap_uint<3> bit3;
typedef ap_uint<2> bit2;
typedef ap_uint<1> bit1;

void BNN( bit16 dim1, bit9 W, bit16* In, bit16* Out);
bit PE(bit9 W, bit9 A);      // process element
```

- BNN.cpp

```
#include "BNN.h"
#define A(i)
(bit9(bit6(bit3(p2(2+i,0+i)).concat(bit3(p1(2+i,0+i))))).concat(bit3(p0(2+i,0+i)))
)

void BNN(bit16 dim1, bit9 W, bit16* input, bit16* output){
#pragma HLS INTERFACE s_axilite port=return
#pragma HLS INTERFACE s_axilite port=dim1
#pragma HLS INTERFACE s_axilite port=weight
#pragma HLS INTERFACE m_axi depth=50 max_widen_bitwidth=32 port=input
```

```

bundle=input_r
#pragma HLS INTERFACE m_axi depth=50 max_widen_bitwidth=32 port=output
bundle=output_r

    bit2 dim;
    bit4 dim1o = dim1-3+1 ;
    bit16 sram_input[16];
    bit16 sram_output[16];
    bit16 p0;
    bit16 p1;
    bit16 p2;
    bit16 conv;

    dim[1] = dim1[4];
    dim[0] = dim1[2];

    loop_input: for(int i=0;i<16;++i){
        if(dim[1]){
            sram_input[i]= input[i];
        }else if(dim[0] & (i<12)){
            sram_input[i]= input[i];
        }else if(i<10){
            sram_input[i]= input[i];
        }
    }
    loop_conv :for(int i=0;i<dim1o+2;++i){
#pragma HLS pipeline II=1
        if(i<dim1){
            p0 = p1;
            p1 = p2;
            p2 = sram_input[i];
        }

        conv[15]=0;
        conv[14]=0;
        conv[13]=(dim[1])? PE(W,A(13) ) : (bit)0;
        conv[12]=(dim[1])? PE(W,A(12) ) : (bit)0;
        conv[11]=(dim[1])? PE(W,A(11) ) : (bit)0;
        conv[10]=(dim[1])? PE(W,A(10) ) : (bit)0;
        conv[9]= (dim[1]|dim[0])? PE(W,A(9) ) : (bit)0;
        conv[8]= (dim[1]|dim[0])? PE(W,A(8) ) : (bit)0;
        conv[7]= (dim[1]|dim[0])? PE(W,A(7) ) : (bit)0;
        conv[6]= PE(W,A(6) );
        conv[5]= PE(W,A(5) );
        conv[4]= PE(W,A(4) );
        conv[3]= PE(W,A(3) );
        conv[2]= PE(W,A(2) );
        conv[1]= PE(W,A(1) );
        conv[0]= PE(W,A(0) );

        if(i>=2){ // 14 2-15 2-11, 2-9
            sram_output[i-2] = conv;
        }
    }
}

```

```

loop_output: for(int i=0;i<dim1o;++i){
    output[i] = sram_output[i];
}
}
bit PE(bit9 W, bit9 A){
    bit9 conv = ~(W^A);
    bit4 sum =
conv[0]+conv[1]+conv[2]+conv[3]+conv[4]+conv[5]+conv[6]+conv[7]+conv[8];
    bit Z = ((sum)>4);
    return Z;
}

```

## 2.2 High Level Synthesis Results

### Performance Estimates

#### Timing

##### Summary

Clock	Target	Estimated	Uncertainty
ap_clk	20.00 ns	14.600 ns	5.40 ns

#### Latency

##### Summary

Latency (cycles)		Latency (absolute)		Interval (cycles)		
min	max	min	max	min	max	Type
32	69	0.640 us	1.380 us	33	70	none

##### Detail

##### Instance

##### Loop

	Latency (cycles)			Initiation Interval			
Loop Name	min	max	Iteration Latency	achieved	target	Trip Count	Pipelined
- loop_input	24	24	10	1	1	16	yes
- loop_conv	3	18	3	1	1	2 ~ 17	yes
- loop_output	0	16	3	1	1	0 ~ 15	yes

Graph 1. Result of high-level-synthesis using Xilinx Vitis\_HLS 2020.2 edition

The input format in prototyping is the NxN matrix, which is slightly different from the spec of this project(NxN matrix + 1 rows indicate dimension).


Also, the protocol of input and output control, AXI Master, is different from this project's spec. Therefore the iteration latency and trip count is a little bit different with RTL design.

The result of high-level-synthesis has pipeline interval = 1, iteration latency = 3. The result means I have three pipe stages in loop\_conv, and the throughput of convolution is 1 row per cycle.

### 3. Interface Specification

#### 3.1 Top Level Interface

Top Level Interface

 

Graph 2. top level interface

#### 3.2 Signal Description

name	source	width	Description
clock	Clock source	1	Global clock signal
reset_b	Reset source	1	Global reset signal, active LOW.

Table 1: global signals

name	source	width	Description
dut_wmem_read_address	BNN	12	index of weight matrix. since TA modified spec and fixed size of weight matrix to, this sram index is fixed at 1.
wmem_dut_read_data	SRAM0	16	Only read weight matrix. weight dimension is fixed to 3.

Table 2: SRAM 0 channel signals


name	source	width	Description
dut_sram_read_address	BNN	12	index of read matrix
sram_dut_read_data	SRAM1	16	read data from read sram, it can be matrix dimension or one row of input matrix

Table 3: SRAM 1 channel signals

name	source	width	Description
dut_sram_write_address	BNN	12	index of wright matrix
dut_sram_write_data	SRAM 2	16	write one row of output matrix to output sram
dut_sram_write_enable	BNN	1	weight data

Table 4: SRAM 2 channel signals

### 3.3 SRAM interface timing diagram

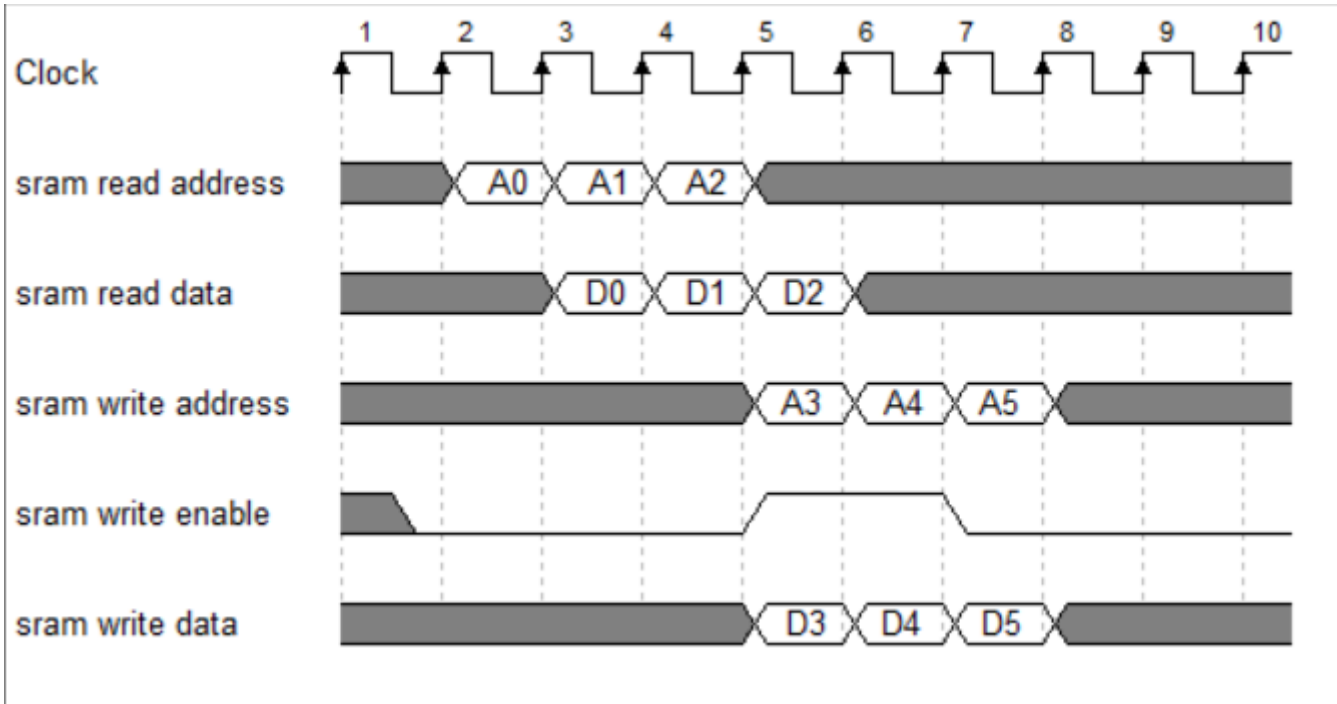

Graph 3. SRAM interface timing diagram

Note: at clock period 7, SRAM write at address A5 failed since SRAM write enable is low.

### 3.4 matrix data format

1. SRAM 1 stores all input matrixes as the following format:

```
@0 1100          // first matrix has 12 rows
@1 1100          // first matrix has 12 columns
@2 00001111111111 // row 0 of matrix 1, zero padding first 4 bits
@3 000011101011001 // row 1 of matrix 1
...
@d 000010101111001 // row 11 of matrix 1
@e 1010          // second matrix has 10 rows
@f 1010          // second matrix has 10 columns
...
```

2. SRAM 0 stores one weight matrix as the following format:

```

@0  11                      // size of weight matrix is fixed at 3.
@1  0000000110101011      // the lowest 9 bits stores weight matrix
// row 0: 011
// row 1: 101
// row 2: 110

```

3. SRAM 2 stores all output matrixes as the following fromat:


```

@0  0011010111010110      // first row of matrix 1
@1  0011110110011011
...
@1f 0000000010110001      // last row of matrix 3

```


## 4. Micro-Architecture

### 4.1 Finite State Machine and Data flow

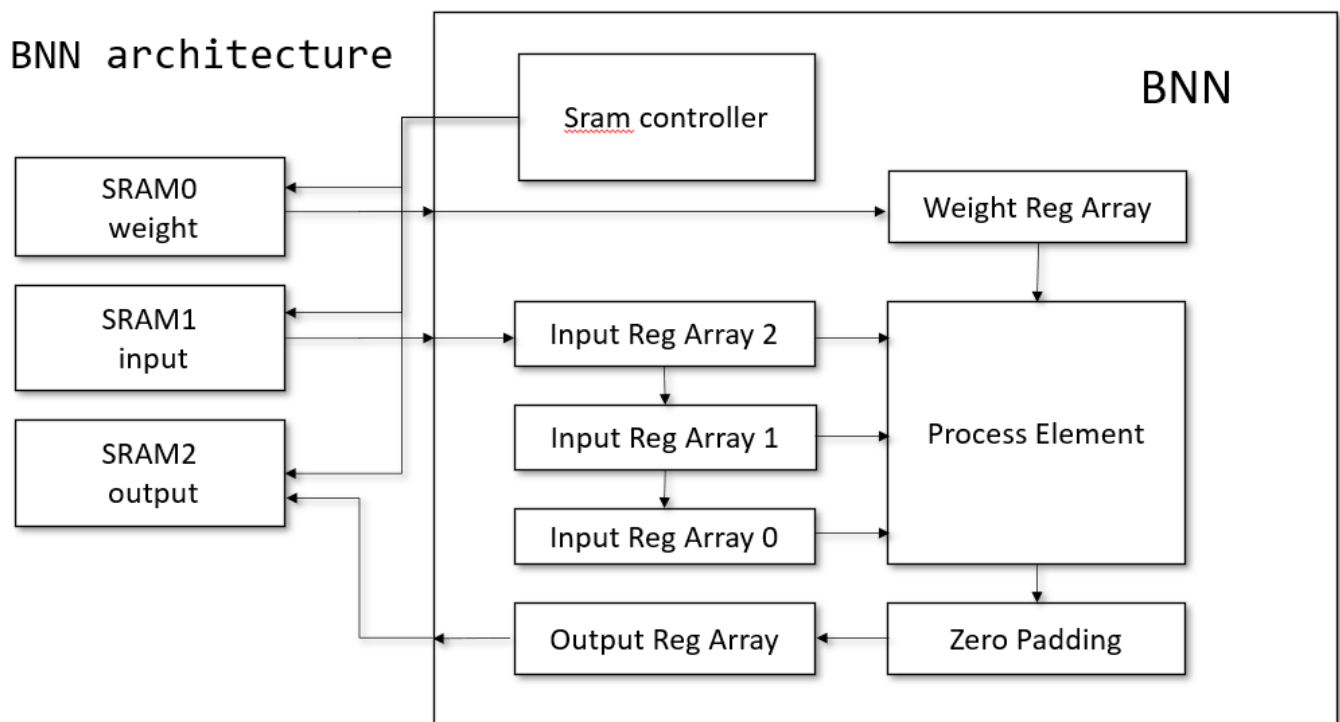

Graph 4. Micro-architecture block diagram



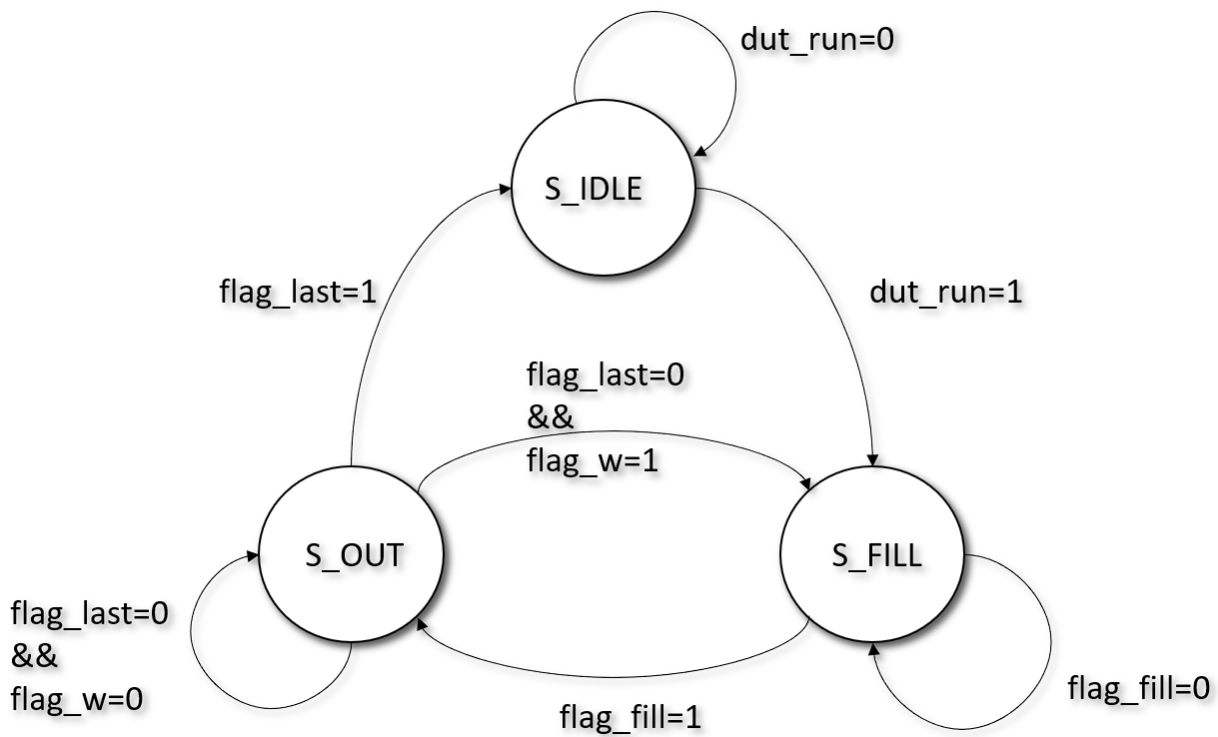

Graph 5. FSM block diagram.

Note: `flag_w` means write done.

1. Control logic:


- SRAM controller
- Finite State Machine: mealy machine

2. Data flow:

- First, store SRAM data in four register arrays.
- Second, use the value of the register array to do binary convolution in the process element.
- Third, zero-padding the result of binary convolution according to matrix's dimension.
- Fourth, store the result in the output register array and write to the output SRAM.

## 4.2 Four Different Binary Convolution microarchitecture

- microarchitecture 1: one 9-input big adder

 


Graph 6. one 9-input big adder

logic to compare if sum > 5:

```
wire [3:0] sum; // max sum = 9 = 1001
assign sum = conv[0] + conv[1] + conv[2] + conv[3] + conv[4] + conv[5] +
conv[6] + conv[7] + conv[8];
// only 4 possible cases : 0101 0110 0111 1000 1001
assign Z_o = sum[3] | (sum[2]&(sum[1]|sum[0]));
```

- microarchitecture 2: two 4-input medium adders

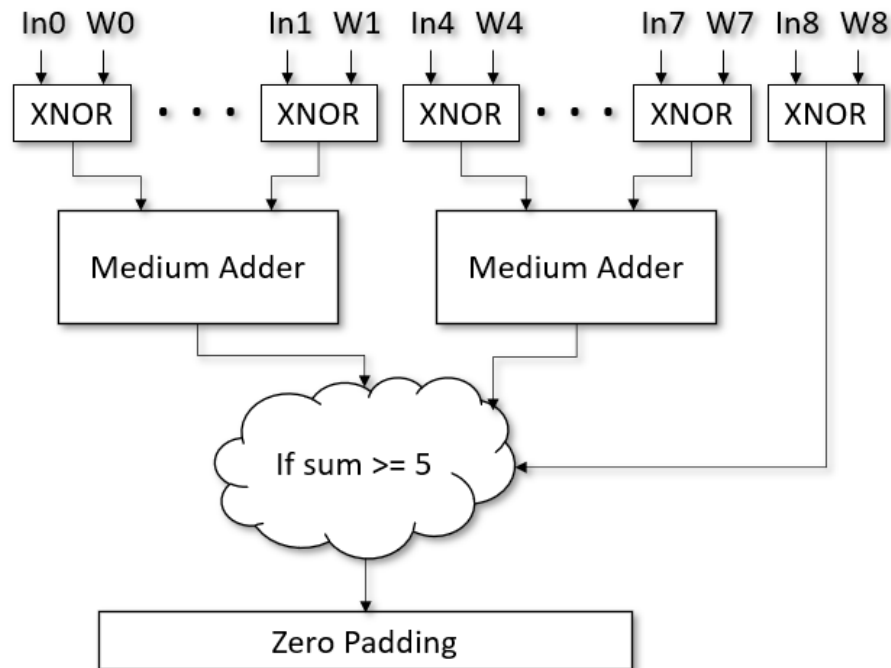

Graph 6. two 4-input medium adders


logic to compare if sum  $\geq 5$ :

```

wire [2:0] sum1;
wire [2:0] sum2;
assign sum1 = conv[0]+conv[1]+conv[2]+conv[3];
assign sum2 = conv[4]+conv[5]+conv[6]+conv[7];
// assume minimum of each (sum1, sum2, conv[8])
// (4,1,x) (1,4,x)
// (3,2,x) (2,3,x)
// (3,1,1) (1,3,1)
// (2,2,1)
assign Z_o =(sum1[2]&((|sum2|conv[8])) |
             (sum2[2]&((|sum1|conv[8])) |
             // (3,2,x) or (3,1,1)
             (sum1[1]&sum1[0] & (sum2[2]|sum2[1]| (sum2[0]&conv[8])) ) ) |
             // (2,3,x) or (1,3,1)
             (sum2[1]&sum2[0] & (sum1[2]|sum1[1]| (sum1[0]&conv[8])) ) ) |
             (sum1[1]&sum2[1]&conv[8]));

```

- microarchitecture 3: three 3-input full adders

 

Graph 7. three 3-input full adders

logic to compare if sum  $\geq 5$ :


```

wire [1:0] sum1;
wire [1:0] sum2;
wire [1:0] sum3;
assign sum1 = conv[0]+conv[1]+conv[2];
assign sum2 = conv[3]+conv[4]+conv[5];
assign sum3 = conv[6]+conv[7]+conv[8];
// all possible case of (sum1,sum2,sum3)
// (sum1>=2,sum2>=2,sum3>=1)
// (sum1>=2,sum2>=1,sum3>=2)
// (sum1>=1,sum2>=2,sum3>=2)
// (3,1,1) (1,3,1) (1,1,3)

assign Z_o = (sum1[1]&sum1[0] & sum2[0] & sum3[0]) | // (3,1,1)
             (sum1[0] & sum2[1]&sum2[0] & sum3[0]) | // (1,3,1)
             (sum1[0] & sum2[0] & sum3[1]&sum3[0]) | // (1,1,3)
             // (sum1>=2,sum2>=2,sum3>=1)
             (sum1[1]&sum2[1] & ((sum1[0]|sum2[0]|sum3[1]|sum3[0])) ) |
             // (sum1>=2,sum2>=1,sum3>=2)
             (sum1[1]&sum3[1] & ((sum1[0]|sum3[0]|sum2[1]|sum2[0])) ) |
             // (sum1>=1,sum2>=2,sum3>=2)
             (sum2[1]&sum3[1] & ((sum2[0]|sum3[0]|sum1[1]|sum1[0])) );

```

- microarchitecture 4: four 2-input half adders

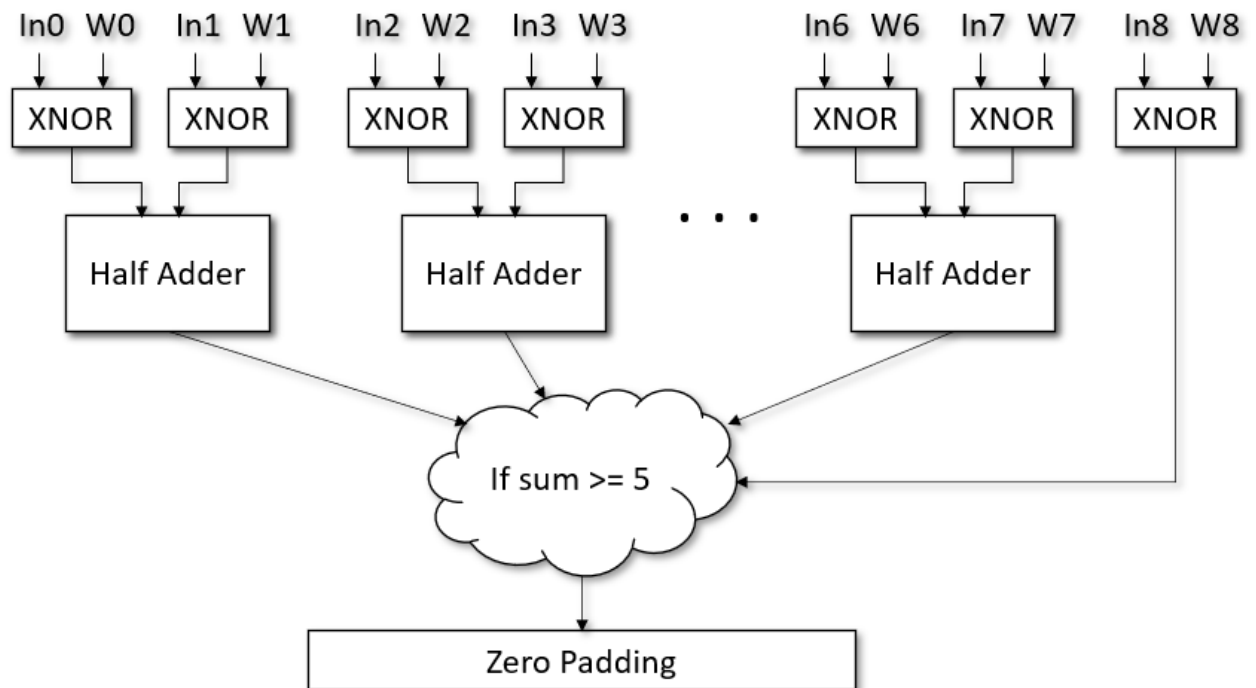

Graph 8. four 2-input half adders

logic to compare if sum  $\geq 5$ :

```

wire [1:0] sum1;
wire [1:0] sum2;
wire [1:0] sum3;
wire [1:0] sum4;
assign sum1 = conv[0]+conv[1];
assign sum2 = conv[2]+conv[3];
assign sum3 = conv[4]+conv[5];
assign sum4 = conv[6]+conv[7];

// assume minimum of each (sum1,sum2,sum3,sum4,conv[8])
// (2,2,1,0,*0), *conv[8] can only be 1 or 0.
// (2,1,1,1,*0)
// (1,1,1,1,*1)
assign Z_o =
// 6 combination of 2,2,1,0,*0
(sum1[1]&sum2[1] & (sum3[1]|sum3[0]|sum4[1]|sum4[0]|conv[8])) |
(sum3[1]&sum4[1] & (sum1[1]|sum1[0]|sum2[1]|sum2[0]|conv[8])) |
(sum1[1]&sum3[1] & (sum2[1]|sum2[0]|sum4[1]|sum4[0]|conv[8])) |
(sum1[1]&sum4[1] & (sum3[1]|sum3[0]|sum2[1]|sum2[0]|conv[8])) |
(sum2[1]&sum3[1] & (sum1[1]|sum1[0]|sum4[1]|sum4[0]|conv[8])) |
(sum2[1]&sum4[1] & (sum3[1]|sum3[0]|sum1[1]|sum1[0]|conv[8])) |
// 12 combination of 2,1,1,1,*0
(sum1[1]&(sum2[0]&sum3[0]&sum4[0])) |
(sum1[1]&(sum2[0]&sum3[0]&conv[8])) |
(sum1[1]&(sum2[0]&sum4[0]&conv[8])) |

```

```

(sum1[1]&(sum3[0]&sum4[0]&conv[8])) |

(sum2[1]&(sum1[0]&sum3[0]&sum4[0])) |
(sum2[1]&(sum1[0]&sum3[0]&conv[8])) |
(sum2[1]&(sum1[0]&sum4[0]&conv[8])) |
(sum2[1]&(sum3[0]&sum4[0]&conv[8])) |

(sum3[1]&(sum1[0]&sum2[0]&sum4[0])) |
(sum3[1]&(sum1[0]&sum2[0]&conv[8])) |
(sum3[1]&(sum1[0]&sum4[0]&conv[8])) |
(sum3[1]&(sum2[0]&sum4[0]&conv[8])) |

(sum4[1]&(sum1[0]&sum2[0]&sum3[0])) |
(sum4[1]&(sum1[0]&sum3[0]&conv[8])) |
(sum4[1]&(sum1[0]&sum2[0]&conv[8])) |
(sum4[1]&(sum2[0]&sum3[0]&conv[8])) |
// 1,1,1,1,1
(sum1[0]&sum2[0]&sum3[0]&sum4[0]&conv[8]);

```

## 5. Verification

---

### 5.1 Generate test pattern

#### 1. generated input sequences

- random weight matrixes
- random input matrixes
- Total 6 order


```

Oder 1: 16x16, 12x12, 10x10
Oder 2: 16x16, 10x10, 12x12
Oder 3: 10x10, 16x16, 12x12
Oder 4: 10x10, 12x12, 16x16
Oder 5: 12x12, 16x16, 10x10
Oder 6: 12x12, 10x10, 16x16

```

#### 2. generated golden output sequence using high-level prototype C model

## 5.2 Test Environment

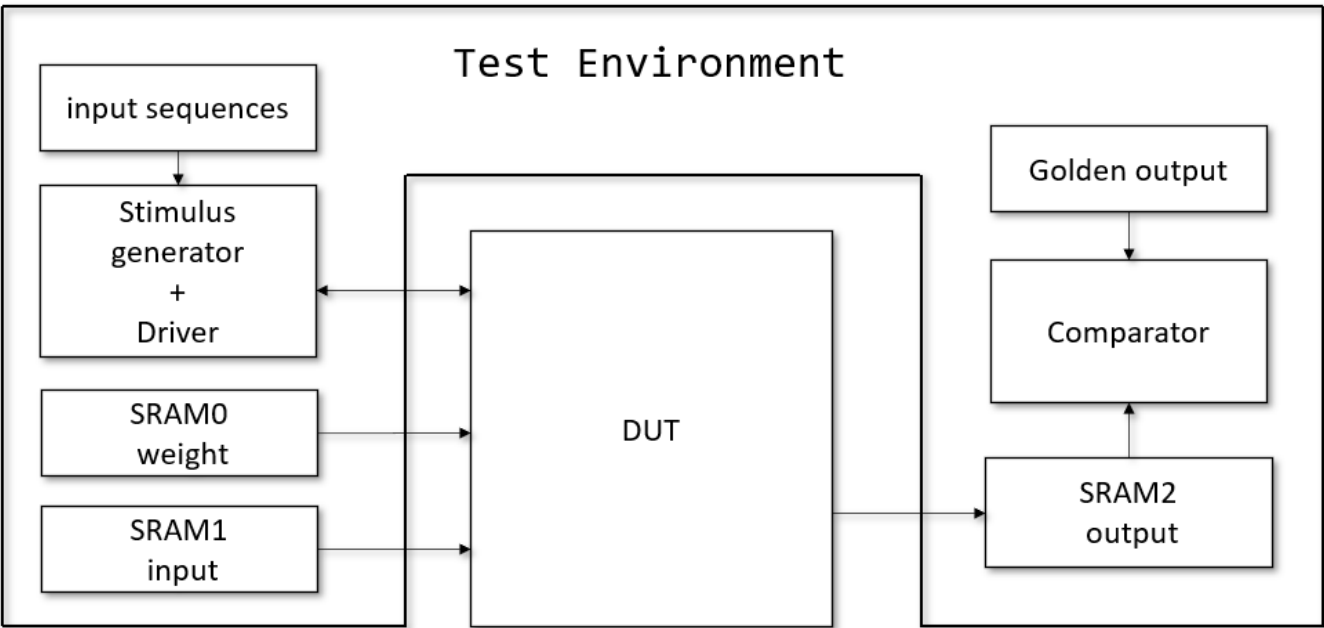

Graph 9. block diagram of the test environment

## 6. Synthesis Results Achieved

### 6.1 My Synthesis flow

1. pick the fastest microarchitecture.

In Table 5, microarchitecture 3, three full adders have the fastest critical path. Therefore I selected this microarchitecture and continued to synthesize and optimization.

---	algo1	algo2	algo3	algo4
clock period(ns)	10	10	10	10
Slack	5.64	6.25	6.29	5.73

Table 5: Slack of four different algorithms

2. develop scripting to automatically synthesis

The script will automatically synthesize from clock "X""1" to "X""9". For example, if we set "X" as "2.4", it will synthesize from clock period 2.41 to 2.49. Also, it merges each netlist's setup-time slack, hold-time slack, total cell area into one single file.

Another script can grab error and warning messages automatically from dc\_shell.log

3. analysis result, try different coding styles, and go back to step 2.

## 6.2 Synthesis Steps

### 1. setup

Script setup parameters such as clock period, top module names, Verilog file directory, report file directory.

### 2. read

Script read Verilog files.

### 3. constraint

Script setup constraints such as clock uncertainty, register clock to Q delay, input port delay, output port delay

### 4. set\_optimized\_registers true (optional)

I will discuss this technique in chapter 6.3.

### 5. compile\_ultra

### 6. optimized\_netlist -area (optional)

I will discuss this technique in chapter 6.3.

### 7. Analysis

Script check\_design, translate to fastest process corner and fixed potential hold time violation., translate back to slowest process corner and fixed potential setup violation.

### 8. output files

Script output Netlist file, area report, max/min timing reports, SDF(standard delay format) files

## 6.3 Techniques for Performance Area Optimization

### 1. Optimizing Critical Path

The critical path is sensitive to clock period and affects cell area significantly. In this project, a critical path occurs at process element(PE) submodules. Therefore, microarchitecture decides the length of the critical path and how fast clock frequency our design can reach.

---	algo1	algo2	algo3	algo4
clock period(ns)	10	10	10	10
Slack	5.64	6.25	6.29	5.73

Table 5: Slack of four different algorithms

The result shows that smaller and parallelized adders have a shorter critical path. However, the overhead of comparing the output signal of adders increases when we increase parallelizing. Therefore, the best microarchitecture is maximum parallelizing adders with only a slight increase in signals that need comparison in non-parallelized logic.



## 2. Optimizing Non-Critical Path:

However, non-critical paths don't have critical paths characteristic. I can't find a clear relation between non-critical paths and cell areas. For example, I tried two different coding styles in part of logic and remained all the rest. The two coding styles show as follows:

case 1. cell area: 1394

```
assign flag_w_n = (dim[1])? (cnt_w==4'd13)
                  : (dim[0])? (cnt_w==4'd9)
                  :          (cnt_w==4'd7);
```

case 2. cell area: 1756

```
assign flag_w_n = (dim[1])? cnt_w[3]&cnt_w[2]&cnt_w[0]
                  : (dim[0])? cnt_w[3]&cnt_w[0]
                  :          &cnt_w[2:0];
```

	case 1	case 2
clock period(ns)	2.44	2.44
cell area	1394	1756

Table 6. comparing cell area of two different coding style

In case 1 operator "==" compares 4 bits. In case 2, I only use two AND gates for each comparison. However, the cell area of case 1 is much smaller than case 2. I guess Synopsys Design Compiler automatically chooses some DesignWareIP in case 1, or it luckily finds a way to optimize the compare logic with another part. In conclusion, this result is unexpected and uncontrolled by coding style. The only way I can optimize non-critical paths is to try all the possible coding styles (sharing logic, pipelining, bitwise operation ..., etc.) and hope one of them works.

## 3. Optimizing Registers

Use synthesis command: `set_optimized_registers true` before `compile_ultra`

This command lets Design Compiler select faster register cells and achieve the fastest clock period. However, register optimization will lead to a huge cell area and got a medium overall performance. Moreover, some lucky case in non-critical path optimization that has smaller cell area does not occur when I compile with the register optimization command. Eventually, I gave up using the register optimization synthesis command.

set_optimized_registers	true	true	false
clock period(ns)	2.19	2.44	2.44
cell area	1776	1700	1394
cycles	44	44	44
$(clk * cycle * area)^{-1}$	5.84e-6	5.48e-6	6.68e-6

Table 7. comparing performance and cell area with/without optimizing registers.

#### 4. Optimizing Netlist Area

Use synthesis command: `optimize_netlist -area` 1. after compile\_ultra 2. before fix potential hold-time violation. The `optimize_netlist -area` command performs monotonic gate-to-gate optimization to improve area without degrading timing or leakage.

<b>set_optimized_registers</b>	<b>true</b>	<b>false</b>
clock period(ns)	2.44	2.44
cell area	1394	1433

Table 8. comparing cell area with/without optimizing netlist area.

#### 5. Optimizing unnecessary signal reset

For some **internal** pipeline registers, its value can be recovered by itself during pipelining. Therefore it is safe to use non-reset Flip-Flops for these registers.

<b>Optimizing unnecessary reset</b>	<b>true</b>	<b>false</b>
clock period(ns)	2.44	2.44
cell area	1433	1452

## 7. Simulation Result

In this chapter, I will discuss the result of simulation and calculate throughput, including Iteration Latency(IL), Initial Iteration(II), Trip Count(TC).

- Throughput:
  - Throughput is defined as how many rows in matrix are computed per clock cycle.
  - In my RTL design, **throughput = 1** (unit: row/cycle)
- Pipeline Iteration Latency calculation:

<b>Iteration Latency (cycles)</b>	
input	1
convolution	3
output	1
Total	5

Table 9. IL of each pipeline

- Trip Count:

- read rows from input SRAM

Trip count = n row of matrix + 1 dimension = n+1 rows

<b>matrix</b>	<b>Trip Count (cycles)</b>
16x16	17
12x12	13
10x10	11
Total	41

Table 10. TC of matrixes

	<b>latency(cycles)</b>	<b>Iteration Latency</b>	<b>Initial Iteration</b>	<b>Trip Count</b>
16x16	19	3	1	17
12x12	15	3	1	13
10x10	13	3	1	11
Total	43	3	1	41

Table 11. IL, II, TC of convolution pipeline


Since I use mealy machine in my RTL design, I save one clock cycle of the first sram input latency.

**Final latency = convolution latency + output latency = 43+1=44 (cycles)**


**Final Performance = 1/ (clock period \* latency \* area) = 1/(Delay \* area) = 1/(147322) = 0.00000678785 = 6.78785e-6**

	<b>value</b>
clock period(ns)	2.438
latency(cycles)	44
Delay(ns)	107.272
cell area(um)	1373.35
Delay*area	147322
Performance	6.78785e-6


Table 12. final result

 

Graph 10. the waveform of computing 16x16 matrix

 

Graph 11. the waveform of computing 12x12 matrix

 

Graph 12. the waveform of computing 10x10 matrix

## 8. Conclusions

---

The result shows that smaller and parallelized adders have a shorter critical path. However, the overhead of processing the output of adders increases when we increase parallelizing. Therefore, the best microarchitecture is maximum parallelized adders with a slight increase in signals that need to process in non-parallelized comparison.

While we all know that a smaller logic path has better performance, this only happens in a critical path. In non-critical paths, the result shows the relation between logic paths and overall cell area is vague. Sometimes minimizing the logic in non-critical paths even make the overall cell area larger.